

Structural Descriptions Using VHDL

Madhav Desai

January 19, 2018

A structural implementation of the 2-bit adder

 


Figure: Structure

Instance Hierarchy

TwoBitAdder

x1 (XOR2)

x2 (XOR2)

a1 (AND2)

x3 (XOR2)

Structural description of the two-bit adder: the entity stays the same

```
entity TwoBitAdder is
  port(x1,x0,y1,y0: in bit;
        s1,s0: out bit);
end entity;
```

VHDL description of the structured architecture

```
architecture Struct of TwoBitAdder is
    signal w, z: bit;
    component XOR2 is
        port (a, b: in std_ulogic;
              c: out std_ulogic);
    and component XOR2;
    component AND2 is
        port (a, b: in std_ulogic;
              c: out std_ulogic);
    and component AND2;
begin
    x_1: XOR2 port map (a => x0, b => y0, c => s0);
    x_2: XOR2 port map (a => x1, b => y1, c => w);
    a_1: AND2 port map (a => x0, b => y0, c => z);
    x_3: XOR2 port map (a => w, b => z, c => s1);
end Struct;
```

What about XOR2, AND2?

- ▶ Need to describe entity and architecture for XOR2, AND2.
- ▶ Interface must be consistent with components for XOR2, AND2.
- ▶ Architecture can be
 - ▶ Structural: For example XOR2 can be implemented by using AND2 and NOT.
 - ▶ Behavioural: using expressions (formulas) as we did for the first implementation of the two-bit adder.

VHDL code structure: libraries

Use libraries: std, ieee (many others).

Useful types: std_ulogic, std_logic

Defined in library ieee, package std_logic_1164.

```
library ieee;
package std_logic_1164 is
    -- lots of stuff..

    TYPE std_ulogic IS ( 'U', -- Uninitialized
                        'X', -- Forcing Unknown
                        '0', -- Forcing 0
                        '1', -- Forcing 1
                        'Z', -- High Impedance
                        'W', -- Weak      Unknown
                        'L', -- Weak      0
                        'H', -- Weak      1
                        '-'  -- Don't care
                    );

    SUBTYPE std_logic IS resolved std_ulogic;
end package;
```


Building blocks

We will describe some building blocks and how simple building blocks can be assembled to make more complex blocks.

INVERTER

```
library ieee;
use ieee.std_logic_1164.all;
entity inverter is
    port (a: in std_ulogic;
          b: out std_ulogic);
end entity inverter;
architecture Behave of inverter is
begin
    b <= not a;
end Behave;
```

Component package

```
library ieee;  
use ieee.std_logic_1164.all;  
package EE224_Components is  
    component inverter is  
        port (a: in std_ulogic;  
              b: out std_ulogic);  
    and component inverter;  
end package;
```

AND2 gate

```
library ieee;  
use ieee.std_logic_1164.all;  
entity and2 is  
    port (a, b: in std_ulogic;  
          c: out std_ulogic);  
end entity and2;  
architecture Behave of and2 is  
begin  
    c <= a and b;  
end Behave;
```

Add AND2 to component package

```
library ieee;
use ieee.std_logic_1164.all;
package EE224_Components is
    component inverter is
        port (a: in std_ulogic;
              b: out std_ulogic);
    and component inverter;
    component and2 is
        port (a, b: in std_ulogic;
              c: out std_ulogic);
    and component and2;
end package;
```

NAND2 gate constructed out of INVERTER, AND2

```
library ieee;
use ieee.std_logic_1164.all;
library work;
use work.EE224_Components.all;
entity nand2 is
    port (a, b: in std_ulogic;
          c: out std_ulogic);
end entity nand2;
architecture Struct of nand2 is
    signal TMP: std_ulogic;
begin
    agate: AND2 port map (a => a,
                          b => b,
                          c => TMP);
    inv: INVERTER port map (a => TMP,
                            b => c);
end Behave;
```

Add NAND2 to Components

```
library ieee;
use ieee.std_logic_1164.all;
package EE224_Components is
    component inverter is
        port (a: in std_ulogic;
              b: out std_ulogic);
    and component inverter;
    component and2 is
        port (a, b: in std_ulogic;
              c: out std_ulogic);
    and component and2;
    component nand2 is
        port (a, b: in std_ulogic;
              c: out std_ulogic);
    and component nand2;
end package;
```

XOR-gate using NAND2's

```
library ieee;
use ieee.std_logic_1164.all;
library work;
use work.EE224_Components.all;
entity xor2 is
    port (a, b: in std_ulogic;
          c: out std_ulogic);
end entity xor2;
architecture Struct of nand2 is
    signal U,V,W: std_ulogic;
begin
    n1: NAND2 port map (a => a, b => b, c => U);
    n2: NAND2 port map (a => a, b => U, c => V);
    n3: NAND2 port map (a => b, b => U, c => W);
    n4: NAND2 port map (a => V, b => W, c => c);
end Behave;
```


What will be the instance hierarchy?

```
xor2
  n1
    agate (1 driver)
    inv   (1 driver)
  n2
    agate (1 driver)
    inv   (1 driver)
  n3
    agate (1 driver)
    inv   (1 driver)
  n4
    agate (1 driver)
    inv   (1 driver)
```

Multiplexor

```
library ieee;
use ieee.std_logic_1164.all;
use work.EE224_Components.all;
entity mux2 is
    port (a, b, sel: in std_ulogic;
          c: out std_ulogic);
end entity mux2;
architecture Behave of mux2 is
begin
    c <= a when (sel = '1') else b;
end Behave;
```

2-4 Decoder

```
library ieee;
use ieee.std_logic_1164.all;
use work.EE224_Components.all;
entity decoder2x4 is
    port (s1, s0: in std_ulogic;
          d3,d2,d1,d0: out std_ulogic);
end entity decoder2x4;
architecture Behave of decoder2X4 is
begin
    d3 <= s1 and s0
    d2 <= s1 and (not s0);
    d1 <= (not s1) and s0;
    d0 <= (not s1) and (not s0);
end Behave;
```

Reality check

Can we routinely describe any combinational circuit in VHDL?

- ▶ Either by transcribing Boolean formulas using concurrent assignments.
- ▶ Or by instantiating gate level network.
- ▶ Or a combination of the two.
- ▶ Or..

A generic test-bench

- ▶ Prepare a trace-file which contains a list of input vectors and expected outputs.
- ▶ The generic testbench reads the trace-file, applies inputs to the device under test (DUT), and checks the outputs against what is expected.
- ▶ The generic testbench can be customized to your specific example.
- ▶ You need to produce the trace-file!

Useful reading material

- ▶ D. Perry, “VHDL Programming by Example”, Tata McGraw-Hill.
- ▶ P. Ashenden, “A VHDL Tutorial”,
hep.uchicago.edu/~tangjian/SVT_sub/FTK_ATLAS/.../vhdl-tutorial.pdf.